

Circuit Simulation Project

<https://esim.fossee.in/circuit-simulation-project>


Name of the participant : Suthar Dhruvi Dilipkumar

Title of the circuit : Octal to Binary encoder

Theory/Description :

An octal to binary encoder consists of 8 input lines and 3 output lines. Each input line corresponds to each octal digit and three outputs generate corresponding binary code.

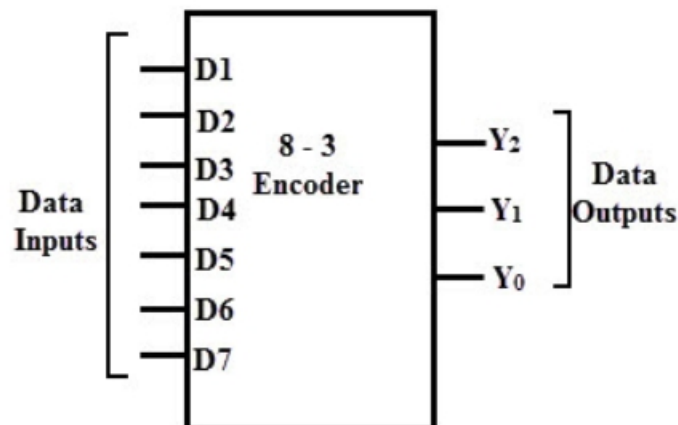In encoders, it is to be assumed that only one input is active or has a value 1 at any given time otherwise the circuit has no meaning. The figure below shows the logic symbol of octal to binary encoder along with its truth table.



Truth table:

No	Inputs								Outputs		
	D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	Y ₂	Y ₁	Y ₀
0	0	0	0	0	0	0	0	1	0	0	0
1	0	0	0	0	0	0	1	0	0	0	1
2	0	0	0	0	0	1	0	0	0	1	0
3	0	0	0	0	1	0	0	0	0	1	1
4	0	0	0	1	0	0	0	0	1	0	0
5	0	0	1	0	0	0	0	0	1	0	1
6	0	1	0	0	0	0	0	0	1	1	0
7	1	0	0	0	0	0	0	0	1	1	1


We can write an equation for Y₂ as mentioned below,

$$Y_2 = D_4 + D_5 + D_6 + D_7$$

Similarly, $Y_1 = D_2 + D_3 + D_6 + D_7$ and

$$Y_0 = D_1 + D_3 + D_5 + D_7$$

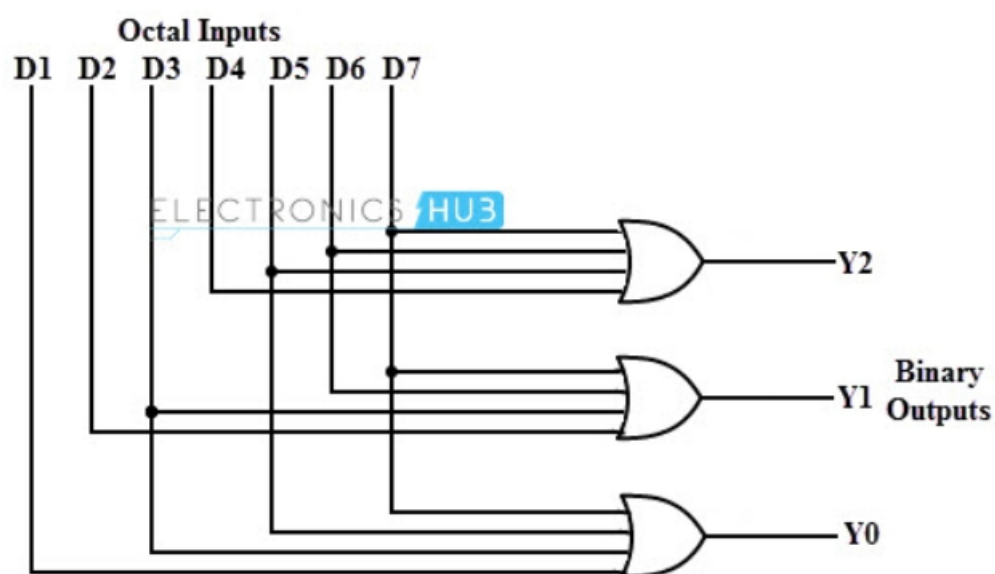
As D₀ doesn't consider in any of the equation, we can consider it as Don't care by considering D₀ as don't care we can implement circuit using OR gates as shown below,



if we give 0 to all inputs, we will be getting 0 as an output. Either D0 is 1/0 .

Results (Input, Output waveforms and/or Multimeter readings) :

Input:

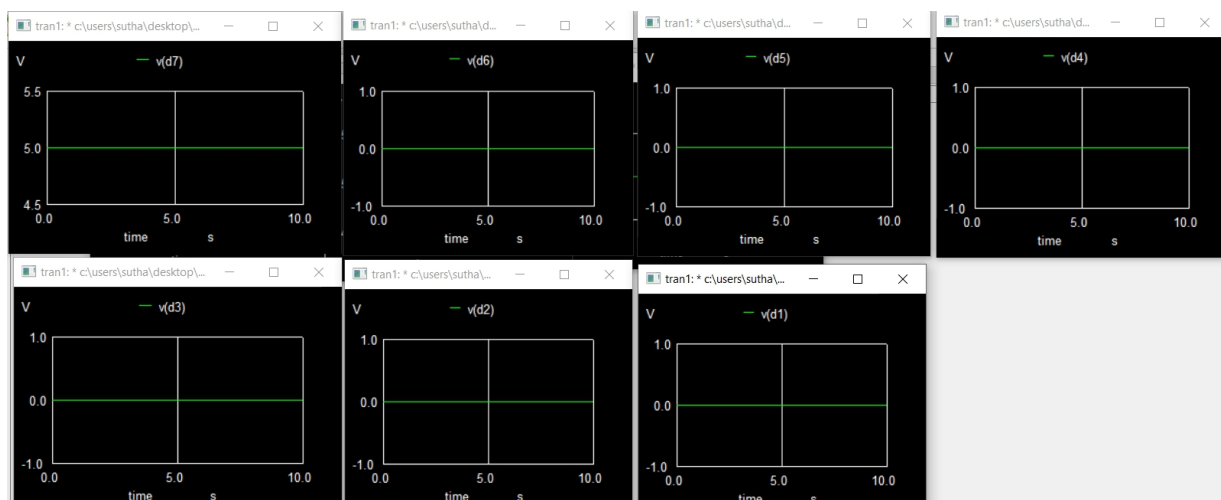

Output:



Source/Reference(s) :

<https://www.electronicshub.org>